

Design of 4-BIT comparator

Mukesh chinta mukeshchinta1313@gmail.com IITH - Future Wireless Communication(FWC22069)

1

1

Contents

- 1 Introduction
- 2 Components
- 3 Hardware
- 4 Implement

- **3.2** connection of pins to the Arduino according to Table 2 and connecting VCC,GND of jumper wires to 5V,GND of Arduino respectively.
- **3.3** Finally, give connections to the arduino and inputs based on table 3.

Input	а	b	С	d	е	f	g	h
Arduino	2	3	4	5	6	7	8	9

Table 3:

Abstract

Design a sequential circuit that take(A3,A2,A1,A0) and (B3,B2,B1,B0) compares both A and B.The o/p should be either one of the (A_iB),(A₂B),(A=B) and it will be displayed by LED's.

1 Introduction

A comparator is an electronic circuit, which compares the two 4-bit inputs that are applied to it and produces an output. The output value of the comparator indicates which of the inputs is greater, lesser or equal.

2 Components

Component	value	quantity		
LED	5V	1		
Arduino	UNO	1		
Jumper wires	M-M	20		
Bread board		1		

Table 1:

3 Hardware



Figure 1: LED.

arduino	2	3	4	5	6	7	8	9	18	19	20
input	a	b	С	d	е	f	g	h			
output									×	у	z

Table 2:

4 Implement

- **4.1** By making Logic circuit based on 4-bit comparator logic we get the circuit as in figure 2.
- **4.2** The code below realizes the 4-bit comparator.

https://github.com/mukeshchinta/FWC_module1/blob/main/fpga-examples/blink/src/main.c

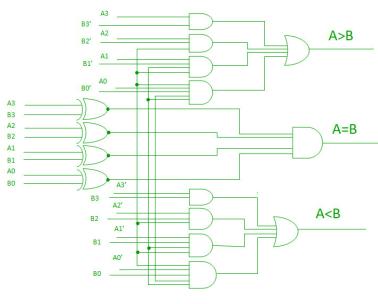


Figure 2